 


## PLL

PLL is closed loop negative feedback system which maintains same phase as the reference signal.

It is used in signal synchronization, communication systems.



## Use of Charge Pump

It is a type of DC-DC converter which uses capacitors to store charge through which it either raises or lowers the voltage levels


Charge Pumps are very important components in the PLL (Phase Lock Loop).

It is used in PLL to convert the error signal generated by the PFD (Phase Frequency Detector) to its equivalent Control voltage which controls the frequency of the VCO.


## Working of CP

A Charge Pump converts the digital UP and DOWN control signals (generated by the Phase-Frequency Detector) into analog currents. These currents are then integrated by the Loop Filter to generate the control voltage for the VCO.


## Basic CP architecture

 

## CMOS Current Mirror CP

 

## Schematic

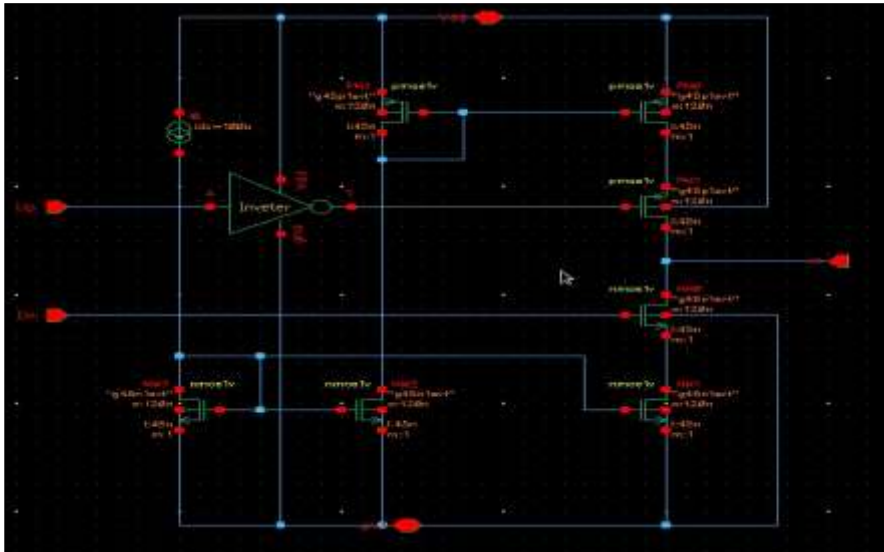

## Charge-Pump Design Steps

### Stage-1: Build Build

1. Set  $I_{CP}$ :  $I_{CP}(100 \mu A)$ , target  $V_{OV} \approx 0.12 V$  for mirrors.
2. Match Transistors: size DN NMOS to sink  $I_{CP}$ ; size UP PMOS  $\approx 1.8-2 \times$  NMOS width so  $I_{UP} = I_{DN}$ .
3. Cascodes (fixed-bias): add simple cascodes above/below mirrors to raise  $r_o$ .

### Stage-2: Values refinement

4. Lengthen mirrors:  $L=0.10-0.12 \mu m$  for increased current driving ability. scale W to keep  $I_{CP}$ .
5. Re-trim  $I_{CP}$ : if current shifted, scale all mirror widths by a single factor.

### Stage-3: Tiny optimization (optional)

6. Series-R @  $V_{CTRL}$ :  $\sim 150 \Omega$  (sweep  $100-300 \Omega$ ) to cut kick/ripple;
7. Bleed ( $1-2 \mu A$ ) PMOS diode to reduce dead-zone;
8. Dummies ( $0.5 \times$ ) pass FETs with complementary gate to cancel charge injection.

## Targets to be achieved:

$\Delta I/I \leq \sim 1-1.5\%$  over  $V_{CTRL}$ .

Ripple  $\lesssim \sim 5 mV_{pp}$ .

similar UP/DN delays (UP branch delay  $\approx$  DOWN branch delay).

## **References**

1. Razavi, B. "Design of CMOS Phase-Locked Loops," *IEEE Circuits & Devices Magazine*, 1996 — classic CP-PLL fundamentals (single-ended CP baseline).
2. Riley, T.; Copeland, M.; Kwasniewski, T. "Delta-Sigma Modulation in Fractional-N Frequency Synthesis," *IEEE JSSC*, 1993 — early PLL with classical charge pump widely cited.
3. Su, D.; Pamarti, S. "Mismatch-Shaping Techniques to Linearize Charge-Pump Errors in Fractional-N PLLs," *IEEE TCAS-I*, 2010 — key treatment of CP mismatch & spur mitigation (background/theory).
4. Noh, J.; Jeong, D. "Charge Pump with a Regulated-Cascode Circuit for Reducing Current Mismatch in PLLs," *ISCAS* — canonical RGC CP idea (motivates why longer-L/ro helps).
5. Wang, Y. et al. "A Wideband Low-Reference-Spur PLL with Clock-Feedthrough-Suppressed Charge Pump," *Electronics*, 2023 — practical low-glitch CP switching tricks (timing/feedthrough).